

EELE 250: Circuits, Devices, and Motors

Lecture 12


Assignment Reminder

- Read 5.1 – 5.4 AND 5.5-5.6
- Practice problems:
 - P5.23, P5.24, P5.35, P5.37
 - P5.42, P5.44, P5.47, P5.49, P5.57
- D2L Quiz #6 by 11AM on Monday 10 Oct.
- REMINDER: Lab #3 report is due and Lab #4 will be performed this week—be sure to do the pre-lab assignment calculations!
- Exam #2: in class on Monday 17 Oct.

Sinusoidal Current and Voltage

- Represent sinusoidal currents and voltages as *phasors*. Length is equal to amplitude, angle is equal to phase (cosine reference).
- Ohm's Law: $V = I \cdot R$, can be generalized to $V = I \cdot Z$, where Z is the *impedance*.
 - Impedance of a resistor: $Z = R$
 - Impedance of an inductor: $Z = j \omega L$
 - Impedance of a capacitor: $Z = 1/(j \omega C)$


Phasors (cont.)

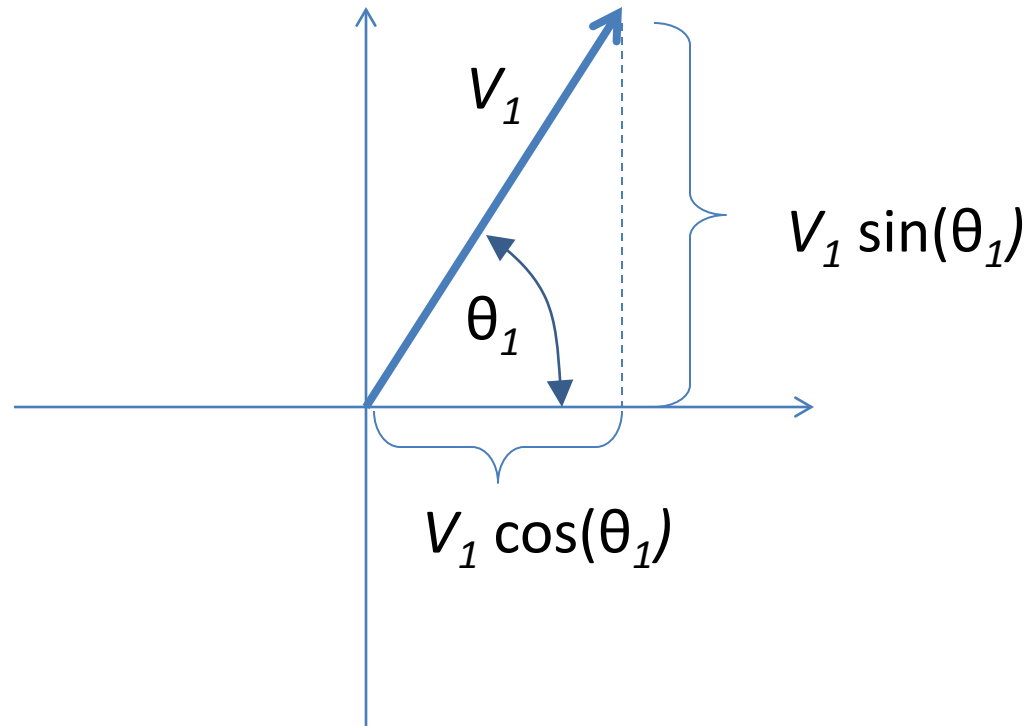


Visualization: Rotating Phasors

- Consider $v(t) = V_m \cdot \cos(\omega t + \theta)$
- Phasor: $V_m \angle \theta$
- We can think of the Phasor as rotating counterclockwise at rate ω radians per second
- Angle at $t=0$ is θ , angle at other times is $\omega t + \theta$
- Rotating Phasor: $V_m e^{j(\omega t + \theta)}$
- $v(t)$ is the real part of the rotating phasor


Rotating Phasors (cont.)

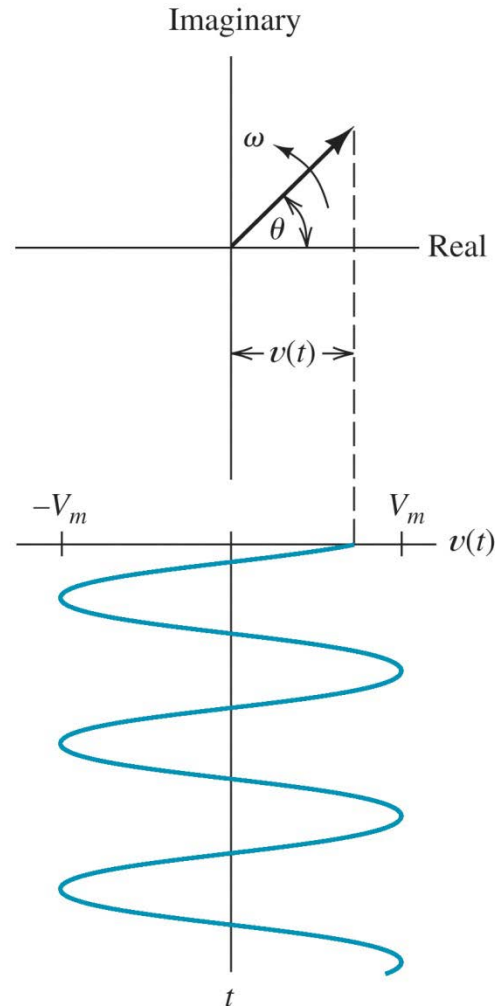

Steady-State AC Analysis

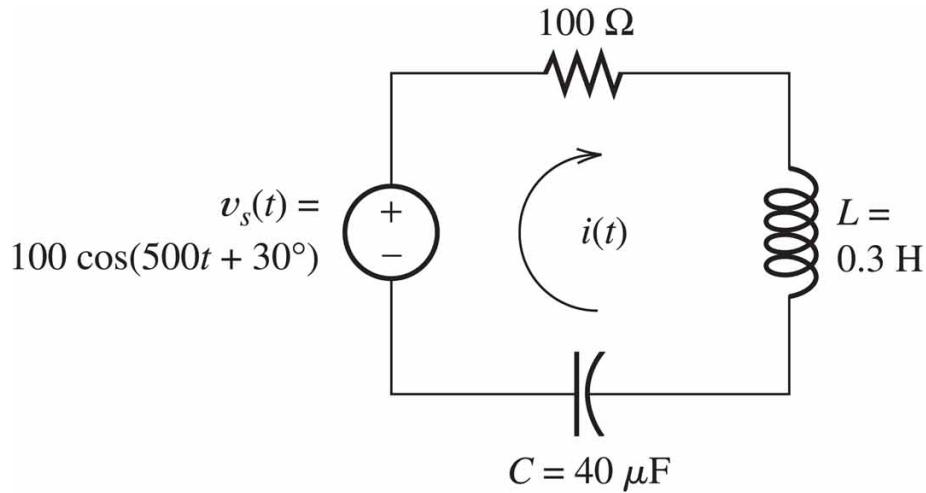

(a)

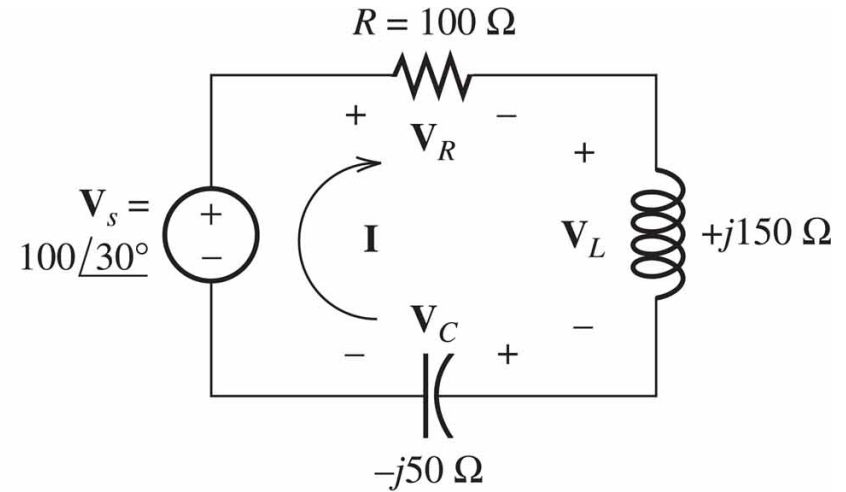


(b)

$$Z_L = j \omega L = j 500 \cdot (0.3) = j 150 \Omega$$

$$Z_C = 1/(j \omega C) = 1/(j 500 \cdot (40\mu)) = 50/j = -j 50 \Omega$$


Phasor Circuit Analysis

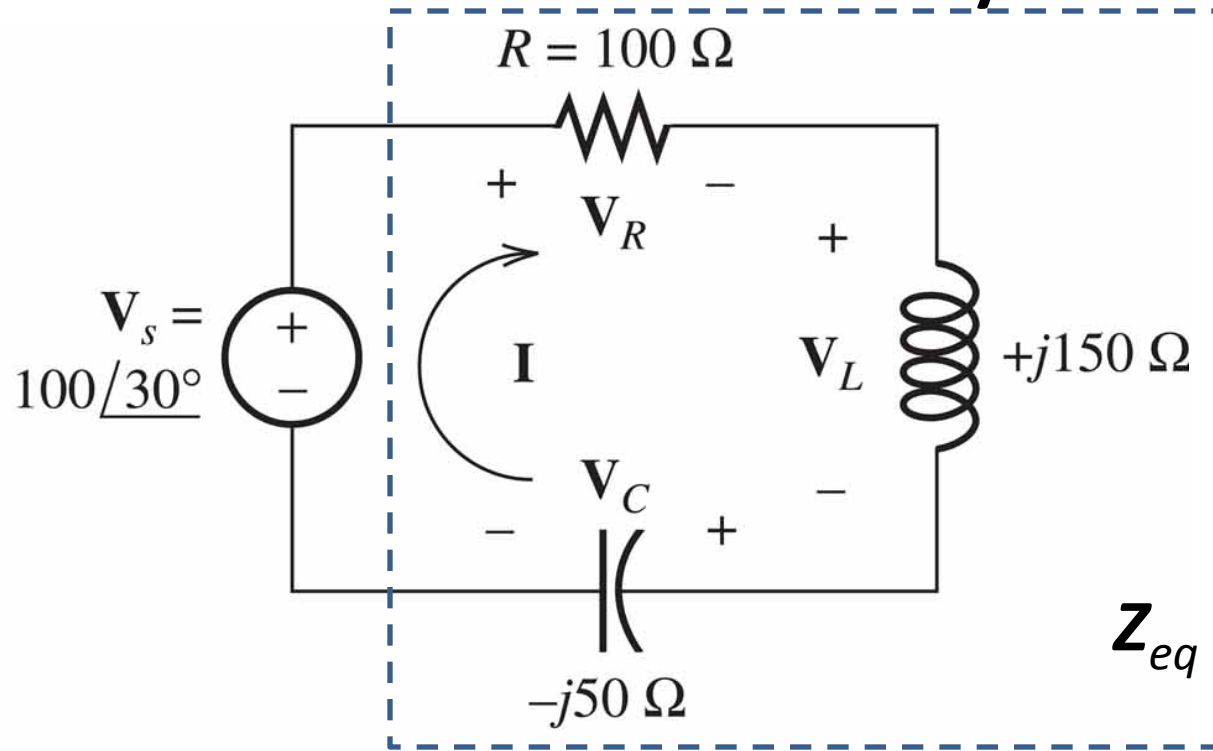

$$\mathbf{Z}_{eq} = 100 + j150 - j50 = 100 + j100 = 141.4 \angle 45^\circ$$

$$\begin{aligned} \mathbf{I} &= \mathbf{V} / \mathbf{Z}_{eq} = (100 \angle 30^\circ) / (141.4 \angle 45^\circ) \\ &= 0.707 \angle -15^\circ \end{aligned}$$

Phasor Analysis (cont.)

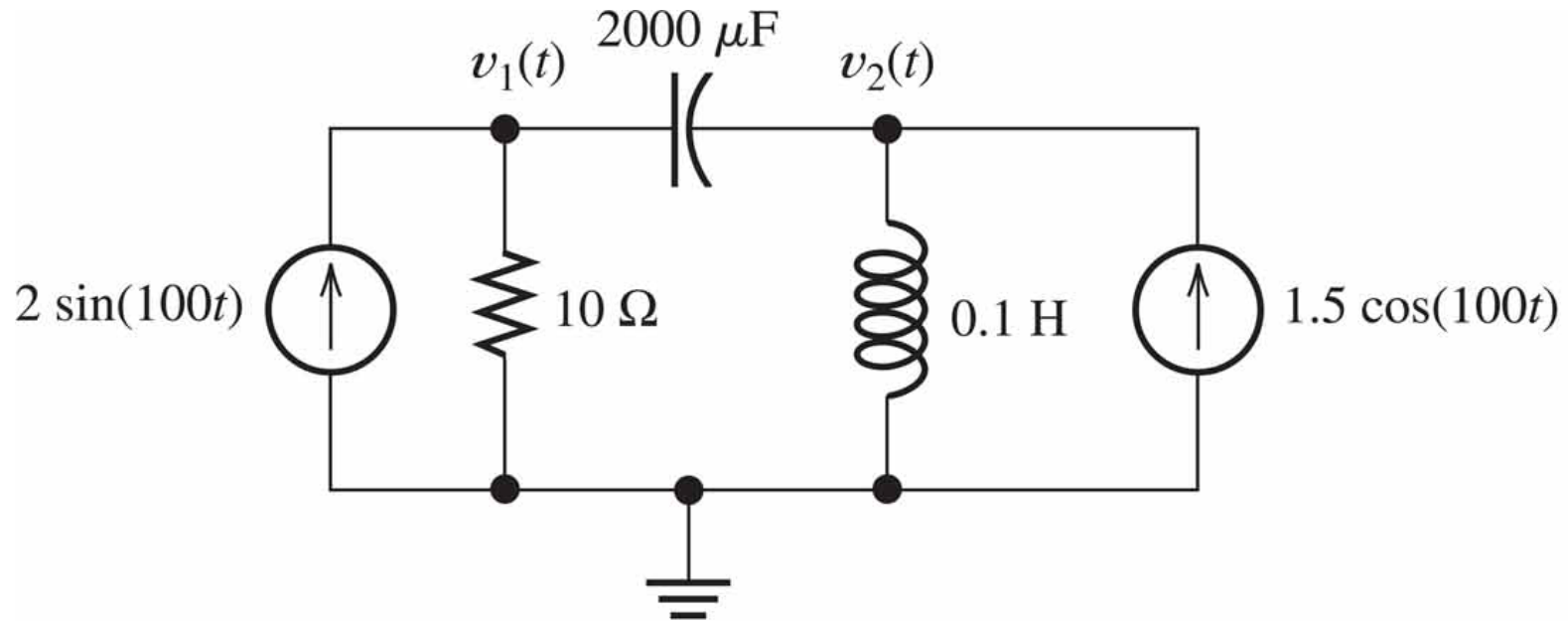

- Convert to impedances
- Write sources and node voltages as phasors
- Write node equations in terms of phasors and impedances
- Solve for phasor voltages, then re-write as time functions

Summary and Review

- Sinusoidal steady-state analysis converts resistors, inductors, and capacitors to impedances, then solve circuit using Ohm's Law, KVL, KCL, Thevenin, etc.
- Impedance of a resistor: $\mathbf{Z} = R$
- Impedance of an inductor: $\mathbf{Z} = j \omega L$
- Impedance of a capacitor: $\mathbf{Z} = 1/(j \omega C)$