

OP-AMPS

Integrators and Differentiators

Integrator

- Integrators produce output voltages that are proportional to the running-time integral of the input voltages. In the running time integral, the upper limit of integration is t .

Integrator Applications

- ▣ Instrumentation
 - ▣ Acceleration signal may be integrated to get signal proportional to velocity
 - ▣ Velocity signal may be integrated to get signal proportional to displacement


- ▣ Extraction of information from digital signals corrupted by noise
 - ▣ Voices - digital phones

Integrator Applications

- ▣ Control systems
 - ▣ Temperature control
 - ▣ Integrate error term
 - ▣ Error term - difference between set-point and actual temperature
 - ▣ Want error term to become zero


- ▣ With integration the error term is sum of instantaneous error over time

Integrator - assume ideal op amp

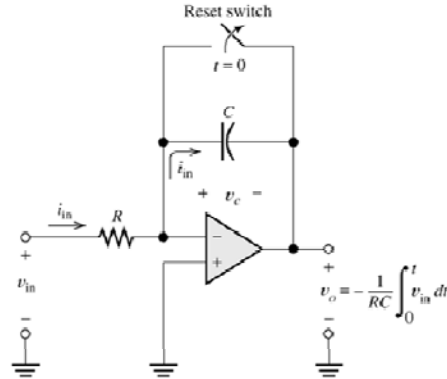

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc
 EELE 250/Fall 2011 Montana State University Sarah Lukes 5

Integrator

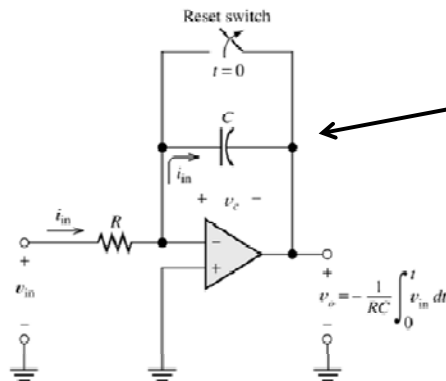


Negative feedback through Capacitor

▣ What is i_{in} ? $i_{in}(t) = \frac{v_{in}(t)}{R}$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc
 EELE 250/Fall 2011 Montana State University Sarah Lukes 6


Integrator

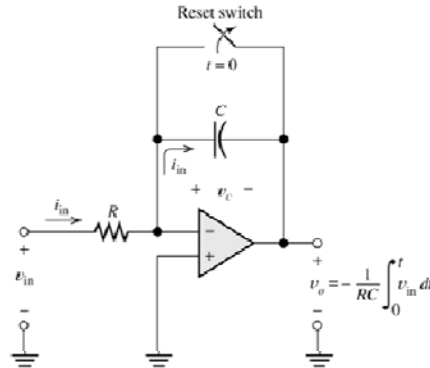

- ▣ What is the capacitor voltage at $t = 0$? 0 V
- ▣ We know $V_- = V_+ = 0 \text{ V}$
- ▣ $V_o(t) + V_c(t) = 0 \Rightarrow v_o(t) = -\frac{1}{RC} \int_0^t v_{in}(t) dt$

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc
 EELE 250/Fall 2011 Montana State University Sarah Lukes 7

Integrator

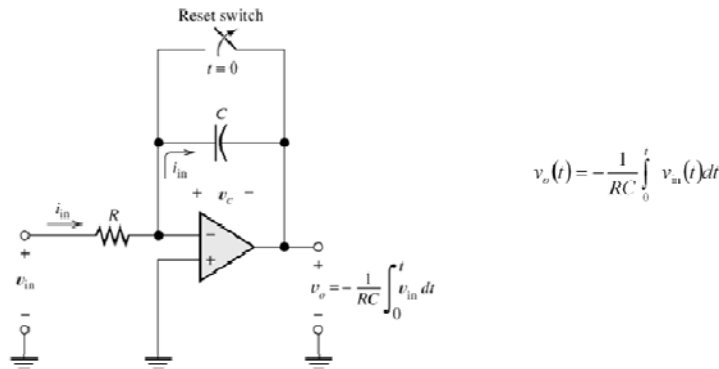

- ▣ V_o is $-1/RC$ times the running integral of the input voltage
- ▣ Choose R and C with gain and bias current in mind
- ▣ Add inverting amplifier if want positive gain

ELECTRICAL ENGINEERING: PRINCIPLES AND APPLICATIONS, Fifth Edition, by Allan R. Hambley, ©2011 Pearson Education, Inc
 EELE 250/Fall 2011 Montana State University Sarah Lukes 8

Differentiator


- ▣ Differentiators produce output voltages that are proportional to the time derivative of the input voltages.
- ▣ Applications
 - Controls
 - ▣ Gives slope of error term over time
 - ▣ Slows the rate of change (reduces overshoot from integrator)
 - ▣ Amplifies noise

EELE 250/Fall 2011

Montana State University

Sarah Lukes 9

Differentiator

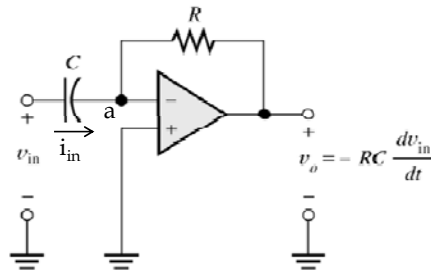

- ▣ Know $V_a = V_+ = 0 \text{ V}$
- ▣ KCL at node a: $i_{in} - \frac{0 - V_o}{R} = 0$

$$V_o = -R * i_{in} = -RC \frac{dv_{in}}{dt}$$

EELE 250/Fall 2011

Montana State University

Sarah Lukes 10

Summary

- ▣ Integrators - output voltages proportional to running-time integral of input voltages.
- ▣ Differentiators - output voltages proportional to time derivative of input voltages.
- ▣ Applications
 - Instrumentation
 - Acceleration \Leftrightarrow Velocity \Leftrightarrow Displacement
 - Control systems