

**\*P14.74.** Sketch the output voltage of the circuit shown in Figure P14.74 to scale versus time. Sometimes, an integrator circuit is used as a (approximate) pulse counter. Suppose that the output voltage is  $-10$  V. How many input pulses have been applied (assuming that the pulses have an amplitude of  $5$  V and a duration of  $2$  ms, as shown in the figure)?


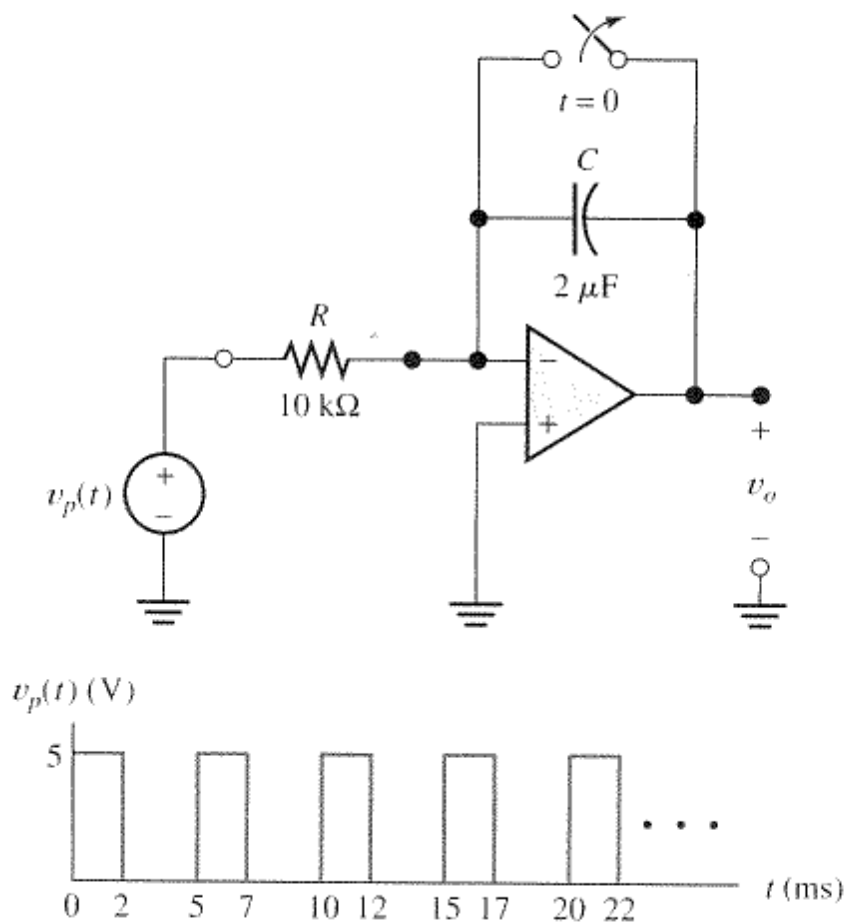


Figure P14.74

**P14.74\*** This is an integrator circuit, and the output voltage is given by:

$$v_o(t) = -\frac{1}{RC} \int_0^t v_{in}(t) dt$$

$$v_o(t) = -50 \int_0^t v_{in}(t) dt$$

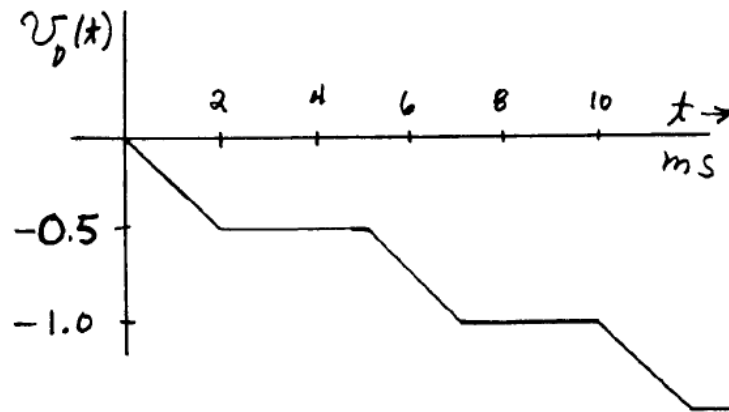

Each pulse reduces  $v_o$  by 0.5 V. Thus, 20 pulses are required to produce  $v_o = -10V$ .

**P14.75.** Sketch the output voltage of the ideal op-amp circuit shown in Figure P14.75 to scale versus time.


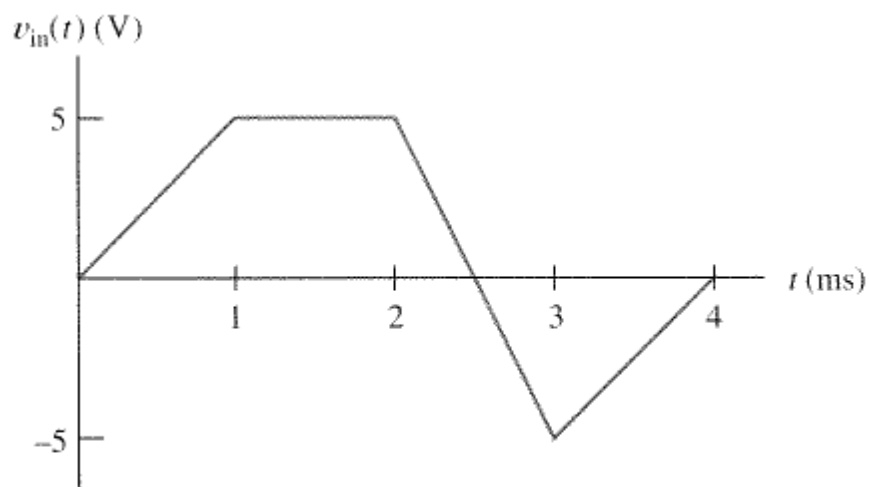


Figure P14.75

**P14.75** This is a differentiator circuit, and the output is given by:

$$\begin{aligned}v_o(t) &= -RC \frac{dv_{in}(t)}{dt} \\ &= -10^{-3} \frac{dv_{in}(t)}{dt}\end{aligned}$$

A sketch of  $v_o(t)$  versus is:

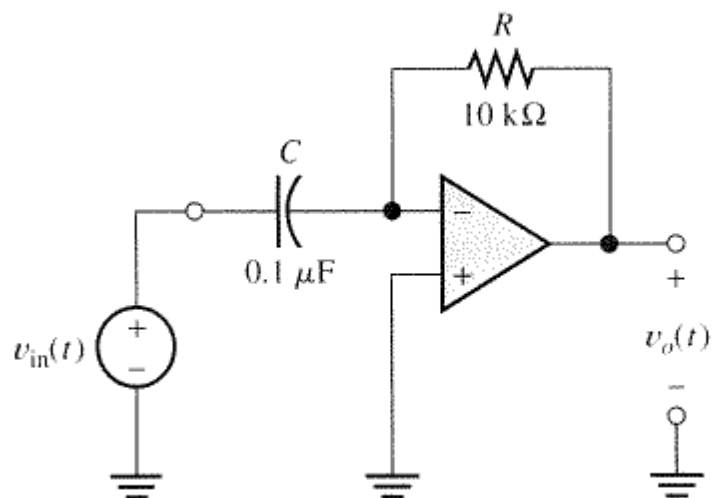